

$$f(C, D, A, B) = CD + DA$$

$$= D \cdot (C+A)$$

Minimal SOP.

2.2

wz

yz	00	01	11	10
00	0	1	1	0
01	x	0	0	1
11	x	0	0	1
10	0	1	1	x

$$f(w, x, y, z) = x\bar{z} + \bar{x}z$$

$$= \underline{x + z}$$

~~graph~~

Note → Technique use for considering min term is important. Always remember this.

2.3

wz

yz	00	01	11	10
00	x	1	0	1
01	0	1	x	0
11	1	x	x	
10	x	0	0	x

$$f(z, w, x, y) = \bar{w}\bar{y} + \bar{z}w\bar{x}$$

$$+ \bar{z}xy$$

No. of literals = 8

Q Which function doesn't implement the K-map?

wz

yz	00	01	11	10
00	0	x	0	0
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

- a) $(w+x)y$ b) $\bar{x}y + y\bar{w}$
 c) $(w+x)(\bar{x}+y)(\bar{w}+y)$ d) None

SOP = $wy + \bar{x}y = y(w+x)$

POS = $(w+y) \cdot (\bar{x}+y)$

Ans → d) None

To verify option c) do each POS term contain two literals so we will cover all zeros with cube size 4, and from given terms in POS we can cover all the 0's.

Finding minimal expression

AB

CD	00	01	11	10	
00	1				→ d
01	1	1	1	1	→ c
11		1	1		→ b
10	1			1	→ a

We have four prime implicants out of which only two are essential and two are redundant.

→ We are going to use prime implicant chart to

	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14
a	1	1	1												
b			1	1							1	1			
c		1	1							1					
d	1	1			1	1									

$$f(ABCD) = \underline{a + b + c/d}$$

Since, c and d both are covering same no. of cubes so we can choose anyone otherwise we will choose the term covering larger no. of cells.

Which of the following can be prime implicant of $f(A, B, C)$

① $ab + c$

				→ Needs
00	01	11	10	2 subcubes
0	1	1	1	
1				

② $bc + \textcircled{a} \rightarrow$ can't possible to denote

00	01	11	10
0	1	1	1
1			

③ $ac + \textcircled{b} \rightarrow$ As above option b also can't display alone

④ $\underline{ab} \rightarrow$ requires 1 subcube.

→ for a prime implicant complete option should lie in a single largest subcube

So, ④ ab is the answer.

Hint → In previous question it is necessary complete option i.e. $(ab+c)$ lies in single subcube. We are not considering ab and c are different.

What min. terms have to be added to make the following function a self dual?

$$f(A, B, C, D) = A'BC + (AC+B)D$$

pair the combination of all possible min. term.

$$(0, 15) (1, 14) (2, 13) (3, 12)$$

$$(4, 11) (5, 10) (6, 9) (7, 8)$$

→ Self dual function doesn't contain mutually exclusive terms.

After expansion we get

$$\Rightarrow A'BC(D+D') + A(B+B')CD + (A+A')B(C+C')D$$

$$\Rightarrow A'BCD + A'B'C'D' + ABCD + AB'C'D + AB'D + ABC'D + A'C'D + A'B'C'D$$

$$\Rightarrow A'BCD + A'B'C'D' + ABCD + (7) \quad (6) \quad (15)$$

$$AB'C'D + A'B'C'D + ABC'D + (11) \quad (5) \quad (13)$$

→ Verify that expression doesn't contain mutually exclusive terms.

→ Add the terms which are not belongs to any pairs.

To make the function self dual we add the two numbers as -

$$(1,3) \quad (14,3) \quad (1,12) \\ (14,12)$$

We can choose any one of the order pair from above 4.

Combining functions having don't cares.

①

$$f(a,b,c) = \sum 0, 2, 4 + \emptyset(3,5,7)$$

$$f_2(a,b,c) = \sum (2,3) + \emptyset(1,6,7)$$

How many functions does $f_1 \cdot f_2$ and $f_1 + f_2$ represents.

Solⁿ

	f_1	f_2	$f_1 \cdot f_2$	$f_1 + f_2$
0	1	0	0	1
1	0	\emptyset	0	\emptyset
2	1	1	1	1
3	\emptyset	1	\emptyset	1
4	1	0	0	1
5	\emptyset	0	0	\emptyset
6	0	\emptyset	0	\emptyset
7	\emptyset	\emptyset	\emptyset	\emptyset

→ \emptyset can hold any value from {0,1} but any value of \emptyset if 'AND' with '0' gives '0' and if 'OR' with '1' gives '1' as outputs

$f_1 \cdot f_2$ have 2 don't cares that can have any value {0,1}

$$\text{So, } 2^2 = 4 \text{ functions.}$$

similarly $f_1 + f_2$ will have $2^4 = 16$ functions.

→ Similarly we can extend this concept upto any no. of variables.

Prime implicants and don't cares

Q The number of prime implicants, essential prime implicants and redundant prime implicants for the function

$$f(A,B,C) = \sum (2,5,6,7) \text{ are } \underline{\hspace{1cm}}$$

Solⁿ

	AB	00	01	11	10
C	0	1	1	1	1
	0				
	1				

No. of prime implicants = 3

No. of essential prime implicants = 2
redundant = 1

Q A function $f(A,B,C) = \sum (3,5,6)$ minimize to $(A+BC)$ then what are the don't cares.

Solⁿ

	AB	00	01	11	10
C	0	1	1	\emptyset	\emptyset
	0				
	1	1	\emptyset	\emptyset	1

$\emptyset = (4,7)$

↓ BC

Poncare should be at 4,7.

Q On a k-map it was found out that essential PI are covering all terms except 2 min terms. Those 2 min terms are in turn covered by 3-non essential prime implicants each.

What is the no. of minimal SOP expressions.

Soln

$$f = EPI + \frac{\text{---}}{3} + \frac{\text{---}}{3}$$

⇒ Total 9 functions are possible.

Excellent Question

In a prime implicant chart representing a boolean expression $f(w,x,y,z)$ columns represent min terms and rows represent Prime Implicants, Identify P,Q,R,S and a,b.

	0	4	5	7	8	a	b
P	✓	✓					
Q	✓			✓			
R		✓	✓				
S		✓	✓	✓		✓	✓

Soln [Solve it self by looking the solution otherwise watch video]

Cox

y_2	00	01	11	10	
00	1	1		1	$P \rightarrow w'y'z'$
01		1	1		$Q \rightarrow x'y'z'$
11		1	1		$R \rightarrow w'xy'$
10					$S \rightarrow xz$

for S if we try to add some more 1 in k-map so that we can form a biggest cube. So that existence of P and R should maintain and also

we can find out a,b.

so,

$$\begin{aligned} a &= 13 \\ b &= 15 \end{aligned}$$

We don't include $a=1$, $b=3$ & $b=0$
a,b are greater than 8 in table.

Variable Entropy Map (VEM)

$$f(A,B,C) = \Sigma(1,2,3,5,6)$$

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

A	B	f
0	0	C
0	1	1
1	0	C
1	1	C'

Behaviour of f on value of A,B.

In (f) section we can choose B instead of 1 but we try to make it simple so choose 1.

A	0	1	
B	C	C	
0	1	C'	
1	1	C'	

→ This way we can reduce the k-map in less no. of variables.

Minimization of VEM

Ex:

AB	00	01	11	10
C	D	I	D'	D'
I	D	I	0	∅

Consider D and D' as the separate variables.

Step 1:

AB	00	01	11	10
C	0	1	0	0
I	0	1	0	∅

$\rightarrow A'B$ (SOP)

\rightarrow Replace D and D' by 0 and find product term.

Step 2 \rightarrow Replace I \rightarrow \emptyset and D by 1 in original k-map, and $D' \rightarrow 0$.

AB	00	01	11	10
C	1	\emptyset	0	0
I	1	\emptyset	0	\emptyset

$\rightarrow A' [A'D]$

Step 3 Replace I \rightarrow \emptyset , D \rightarrow 0 and $D' \rightarrow 1$ in original k-map

AB	00	01	11	10
C	0	\emptyset	1	1
I	0	\emptyset	0	\emptyset

$\Rightarrow AC' + A'D + A'C'D'$

Procedure:

① Set all the variables in the cell as 0's and obtain SOP expressions.

② a) Make one variable in the cell as 1, and obtain SOP by making earlier minterms (1's) as don't cares.

b) Multiply the above SOP with concern variables

③ Repeat the step 2 until all the variables in the cells are covered.

④ SOP of VEM is obtained by (ORing) the previous SOP expressions.

Ex $\rightarrow f(A,B,C) = \Sigma(3,5,6,7)$ is realized by following VEM, then find P, Q, R, S.

b	0	1
0	P	S
1	R	Q

a) $P=0, R=S=C, Q=1$

b) $P=Q=0, R=C, S=1$

c) $P=0, R=Q=C, S=1$


d) None

Soln

(VEM) ↴

A	B	C	f	A	B	f
0	0	0	0	0	0	0
0	0	1	0	0	1	C
0	1	0	0	1	0	C
0	1	1	1	1	1	1
1	0	0	0			
1	0	1	1			
1	1	0	1			
1	1	1	1			

P = 0
Q = 1
R = C
S = C

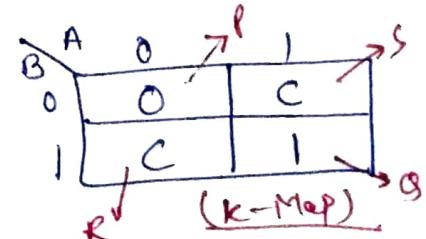

Question was about finding value of P, Q, R, S but we are extending it to find minimal expression.

	0	1
0	0	C
1	C	1

Step 1:

	0	1
0	0	0
1	0	1

ab

Step 2:

	0	1
0	0	1
1	1	0


(a+b)C

Step-3: ab + ac + bc is the minimal expression.

→ It is also a self dual function.

Finding the free variables

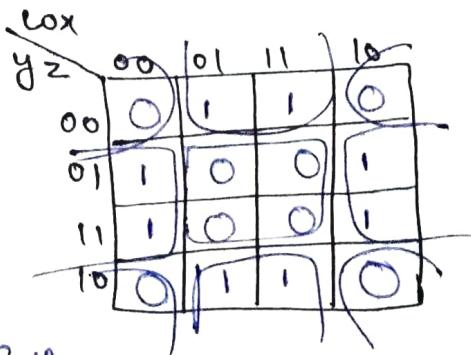How many variables are free in the expression denoted by the following K-map?



Soln

$$f = x\bar{z} + \bar{x}z = x \oplus z$$

→ It depends on only two variables x & z.

→ w, y are free variables.

$$\text{SOP} = x\bar{z} + z\bar{z}$$

$$\text{POS} = (x+z) \cdot (\bar{x}+\bar{z})$$

If SOP depends on two variables POS will also depend on two variables

Relation between POS and SOP in case of don't care

1.

wx	00	01	11	10
yz	00	Q	Q	0
00	0	0	1	1
01	0	0	1	1
11	1	1	1	1
10	0	0	0	0

wz
+
yz

→ If a K-map have n-cells with don't care then total 2^n combinations of functions are possible.

→ We will include don't care if and only if it will provide us the subcube of largest size otherwise not.

→ $f = (wz + yz)$ from above K-map.

→ If we include ϕ (don't care) we consider them as '1' bcz we want to include it in subcubes otherwise we assume it as '0'. [In SOP]

→ In above K-map, we have no need to include ϕ so we assume them as '0'

	01	11
00	0	0

Consider the table given below

$w \times y \times z$	f	f_1	f_2	f_3	f_4
0	0	0	0	0	0
1	0	0	0	0	0
2	0	0	0	0	0
3	1	1	1	1	1
4	∅	0	0	1	1
5	0	0	0	0	0
6	0	0	0	0	0
7	1	1	1	1	1
8	0	0	0	0	0
9	1	1	1	1	1
10	0	0	0	0	0
11	1	1	1	1	1
12	∅	0	1	0	1
13	1	1	1	1	1
14	1	1	1	1	1
15	1	1	1	1	1

We can replace \emptyset as
 $0\ 0, 0\ 1, 1\ 0, 1\ 1$.

As we find the minimal exp.
as $wz + yz$ so we are
not considering this don't
care terms means assuming
both as 0. So we are following
the specific function f_1 .

$\Rightarrow f_1$ is special case of f_0 .

Similarly if we find POS
by considering both \emptyset as 0
then we get,

$$POS = z \cdot (w+y)$$

So, by considering f_1 we get
both minimal POS and SOP.

Ex: 2 Let $f(w,x,y,z)$ is a
function containing (3, 2, 3, 5, 13)
as min. terms and (6, 7, 8, 9, 11, 15)
as don't care and let $g(w,x,y,z)$
be minimized SOP and $g(w,x,y,z)$
is minimized POS. Are f and
 g identical.

SOLⁿ

Cox

y_2	00	01	11	10
00	0	0	0	\emptyset
01	1	1	1	\emptyset
11	1	\emptyset	\emptyset	\emptyset
10	1	\emptyset	0	0

→ for SOP

$$f = \sum (1, 2, 3, 5, 6, 7, 9, 11, 13, 15)$$

Cox

y_2	00	01	11	10
00	0	0	0	\emptyset
01	1	1	1	\emptyset
11	1	\emptyset	\emptyset	\emptyset
10	1	\emptyset	0	0

→ for POS

$$g = \sum (1, 2, 3, 5, 13, 9)$$

Here, 2^6 combinations of functions
are possible due to don't care.
So we can choose any 1 from 64
for minimal SOP and minimal POS.

→ And for 'f' and 'g' be identical
only one function among 64
must satisfy both minimal POS
and SOP.

→ In case of POS, include \emptyset
don't care assumes as '0' and
not includes assumes as '1'.

→ Although 'f' have only one
way to get minimal SOP
but 'g' have many way
to get minimal POS. So both
are not identical.

Comparing independent variables in minimal SOP and POS

Minimal expression represented by map is free from

- 1) 1-variable
- 2) 2variables
- 3) 3-variables
- 4) dependent on all.

AB	00	01	11	10
CD	00	1	0	0
	01	1	1	0
	11	1	1	1
	10	1	1	1

$$SOP = C + \bar{A}D + \bar{A}\bar{B}$$

$$\begin{aligned} POS &= (B\bar{C}\bar{D} + A\bar{C})' \\ &= (B + \bar{C} + \bar{D}) \cdot (A + \bar{C}) \end{aligned}$$


So, Both POS and SOP dependent on all four variables.

Note: If no don't care present in K-map then no. of dependent variable should be same in both both POS and SOP.

Number of irredundant and minimal expression

Question.

- ① No. of prime implicants?

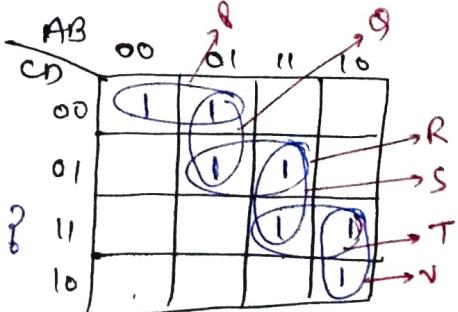

- ⑤ No. of essential prime implicants?
- ⑥ No. of redundant prime implicants?
- ⑦ Minimal SOP?
- ⑧ How many minimal?

SOP

→ 6 prime implicant.

2 essential prime implicant.

4 redundant prime implicant.

Prime implicant chart (Table 1)

	0	4	5	10	11	13	15
P	✓	✓					
Q			✓	✓			
R				✓			✓
S						✓	✓
T					✓		✓
V					✓	✓	

$$P = A'C'D', Q = A'BC'$$

$$R = BC'D, S = ABD$$

$$T = ACD, V = AB'C$$

$$\text{Essential PI} = P + V$$

$\swarrow (0,4)$ $\searrow (10,11)$

So, we need to cover 5, 13, 15 using remaining 4 product terms.

Reduced prime implicant chart

	5	13	15
Q	✓		
R		✓	
S		✓	
T			✓

(Table 2)

$\rightarrow Q$ is dominated by R and T is dominated by S .
It means whatever Q, T includes already includes in R and S but whatever R and S required Q and T are not able to provide.

So, we can remove Q and T bcoz all are of same size.


$$Q \rightarrow R, T \rightarrow S$$

	5	13	15	Table 3
R	✓	✓		
S		✓	✓	

So, minimal expression is $P + V + R + S$.

No. of minimal SOP possible:

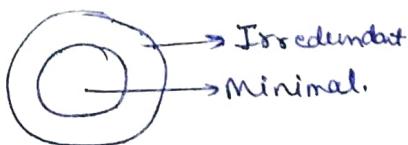Every minimal expression is irredundant but vice-versa is not always true.



from Table ② we can say that to cover

5 we can use Q or R

13 ————— R or S

15 ————— S or T

$$\Rightarrow (Q+R) \cdot (R+S) \cdot (S+T)$$

$$\begin{aligned} \Rightarrow & QRS + QRT + QSS, \\ & QST + RSS + RRT \\ & + RSS + RST \end{aligned}$$

$$\begin{aligned} \Rightarrow & QRS + QRT + QSS + QST \\ & + RSS + RRT + \cancel{QSS} + RST \\ \Rightarrow & QSC(1+R) + RSC(1+T) \\ & + RTC(1+Q) + QST \\ \Rightarrow & QS + RS + RT + QST \\ \Rightarrow & \underline{\underline{QS + RS + RT}} \end{aligned}$$

So, to cover $(S, 13, 15)$ we can use combinations like $(Q, S), (R, S), (R, T)$

So, no. of minimal expression which are irredundant = 3 as,

$$\begin{array}{l} P + V + Q + S \\ P + V + R + S \\ P + V + R + T \end{array} \quad] \quad \underline{\text{3 expression}}$$

\rightarrow So finding no. of minimal exp. is a lengthy process.

Don't care never included in prime implicant chart.

$$f(V, W, X, Y, Z) =$$

$$\sum (13, 15, 17, 18, 19, 20, 21, 23, 25, 27, 29, 31) + \sum \emptyset (1, 2, 12, 24)$$

$$\begin{array}{lll} A = VZ & C = VWX'Y' & E = VWXY'G = W'X'Y'Z \\ B = WXZ & D = VW'X'Y' & F = VWXX'Y' = W'X'Y'Z \end{array}$$

	13	15	17	18	19	20	21	23	25	27	29	31
A		✓		✓		✓	✓	✓	✓	✓	✓	✓
B	✓	✓										
C												
D							✓	✓				
E							✓	✓				
F	✓											
G							✓					
H						✓						

→ Don't care use to find min. terms as prime implicants and prime implicant chart doesn't contain don't care.

function involving functions

Ex 1: Consider the 3-variable functions

$$f_1(A, B, C) = \sum(0, 7) + \sum_{\phi}(1, 2, 5)$$

$$f_2(A, B, C) = \sum(0, 1, 3) + \sum_{\phi}(4, 7)$$

find $f_1 \cdot f_2$ and $f_1 + f_2$ when minimized.

A B C	f_1	f_2	$f_1 + f_2$	$f_1 \cdot f_2$
0 0 0	1	1	1	1
0 0 1	\emptyset	1	1	\emptyset
0 1 0	\emptyset	0	\emptyset	0
0 1 1	0	1	1	0
1 0 0	0	\emptyset	\emptyset	0
1 0 1	\emptyset	0	\emptyset	0
1 1 0	0	0	0	0
1 1 1	1	\emptyset	1	\emptyset

$$\begin{array}{c|cc} & \text{OR} & \text{AND} \\ \hline 1 + \emptyset & 1 & 1 \cdot \emptyset = \emptyset \\ 0 + \emptyset & \emptyset & 0 \cdot \emptyset = 0 \end{array}$$

A B	00	01	11	10
C	1	\emptyset	1	\emptyset
0	1	\emptyset	1	\emptyset
1	\emptyset	1	\emptyset	1

$$f_1 \cdot f_2 = A' B'$$

A B	00	01	11	10
C	1	\emptyset	1	\emptyset
0	1	\emptyset	1	\emptyset
1	1	1	1	\emptyset

$$\rightarrow f_1 + f_2$$

$$\rightarrow f_1 + f_2$$

$$f_1 + f_2 = C + A'$$

$$\rightarrow \text{True}$$

$$f_1 \cdot f_2 = \sum(0) + \sum_{\phi}(1, 2)$$

Note → Do these kind of questions using method only. No need to apply any tricks.

Ex 2: Consider a new boolean operation '\$' defined as $A \$ B = A' + B$ then find

$$f_1 \$ f_2$$

AB		00	01	11	10
C	0	0 1 0 1	0 1 0 1	0 1 0 1	0 1 0 1
0	0	1	0	1	1
1	0	1 1 1 0	1 0 1 1	1 0 1 1	1 0 1 1

A B C	f_1	f_2	$f_1 + f_2$	$f_1 \$ f_2$
0 0 0	0	0	1	1
0 0 1	0	0	0	1
0 1 0	1	0	0	0
0 1 1	1	1	1	1
1 0 0	1	1	1	1
1 0 1	0	1	1	1
1 1 0	0	0	0	1
1 1 1	1	1	1	1

AB		00	01	11	10
C	0	1 0	1 1	1 1	1 1
0	1	\emptyset	1	1	1
1	1	1	1	1	1

$$f_1 \$ f_2 = C + A + \bar{B}$$


→ All three (A, B, C) are essential prime implicants.

Design and Synthesis of Combinational Circuits

Introduction to Logic Design

The main application of switching theory is in design of digital circuits. It is called as logic design.

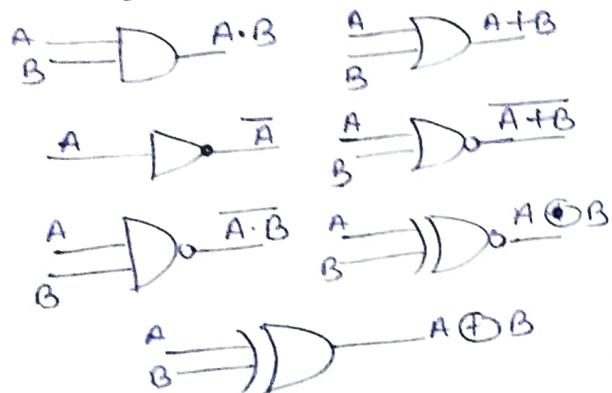→ These circuits are designed using basic elements called gates.



→ In DLD we consider only digital inputs.

→ During design we try to reduce the cost and propagation time (t_p).

→ We can reduce (t_p) by decreasing levels.


→ Gates used in numbers -

- ① < 10 → Small scale Integration
- ② 10 - 100 → Middle
- ③ 100 - 1000 → Large
- ④ > 1000 → VLSI

(AND-OR), (OR-AND) realisation


$$f(A, B, C, D) = AB + CD$$

↳ SOP

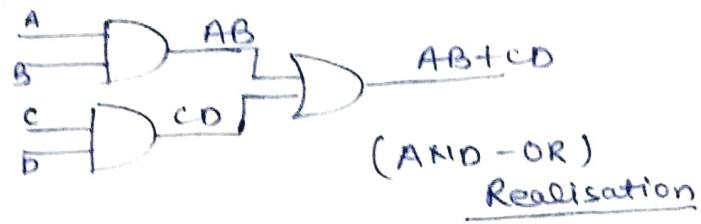

POS

$$f(A, B, C, D) = (A + B)(C + D)$$

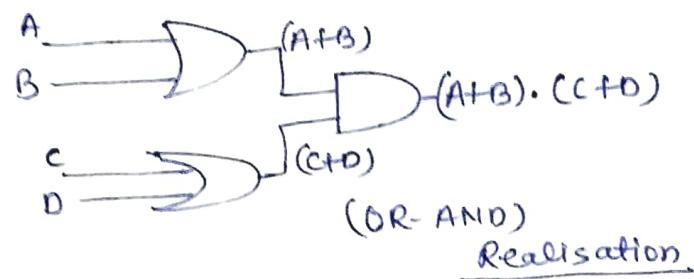


→ Any function can be represented in these two ways.

→ We can represent a function $f'(A, B, C, D)$ in two ways, such that


$$f'(A, B, C, D) = ABC + CD$$

①

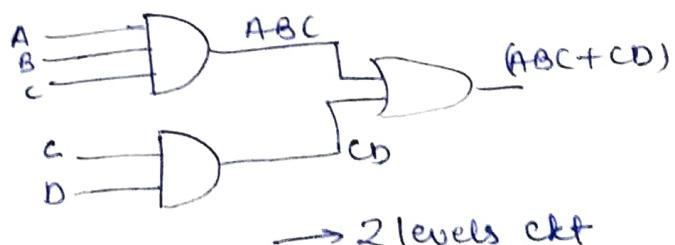



→ 2 levels ckt

②

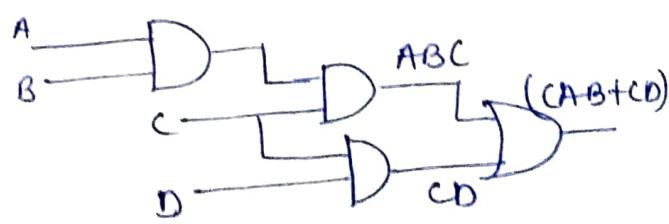

→ 3 level ckt

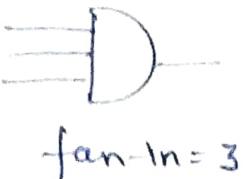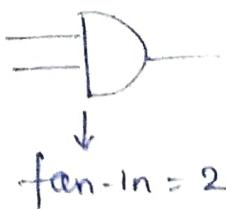→ 2 level ckt is more costly but time is less and 3-level ckt is less costly but propagation time is high.




No. of levels ↑ cost ↓ pt ↑

→ If don't specified anything
Consider fan-in = 2.


Q Why NAND and NOR are
said to be universal
gates?

Ans → Every function can be
either in SOP or POS.

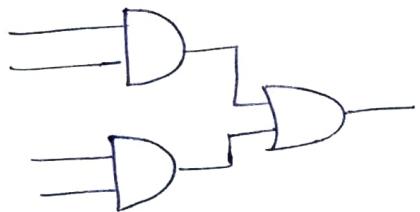We represent SOP as (AND-OR)
realisation and its logic circuit
diagram is




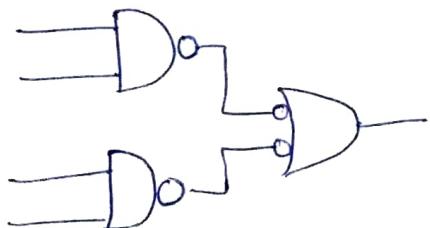If we introduce complement
(bubble) in fig as -



Both figures are same bcoz
we are complementing the digit
at the 0/p end of AND and
at the 1/p end of OR.

→ This diagram can be
further reduce to,

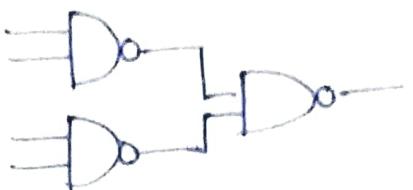

So, (AND-OR) realisation
also called as (NAND-NAND)
realisation.

So, we can represent any
SOP combination using NAND
gates

Similarly we can represent any
POS combination / function
using NOR gate.

→ So, to represent any fn
we need only NAND and
NOR Gates.

NAND → { AND, NOT } : S₁
NOR → { OR, NOT } : S₂


And we already prove
earlier that both S₁ and S₂
are functionally complete.

→ (OR-AND) also called as
(NOR-NOR) realisation.


→ Realisation can be said as
implementation.

→ Hence, we need to manu-
facture only NAND and NOR
gate instead of other gates.

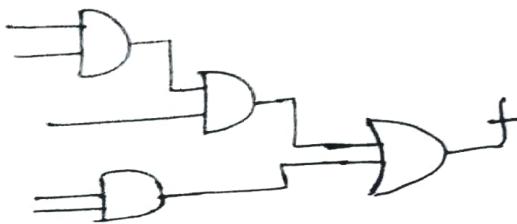Identify min. no. of two 1/p NAND gates required to represent the following



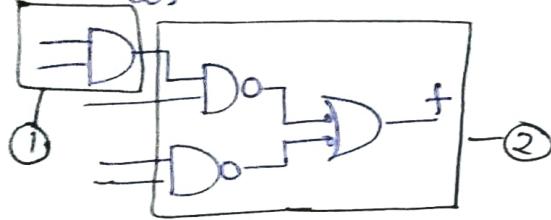Solⁿ Do some changes in (AND-OR) realisation as.



So, ② part can implement using 3 NAND gate, and for ①

$$A \rightarrow \overline{AB} = AB$$


$$A \rightarrow \overline{AB} \rightarrow \overline{\overline{AB}} = \overline{AB}$$

we need 2 NAND gates


→ So we need total

$$(3+2) = 5 \text{ NAND gates.}$$

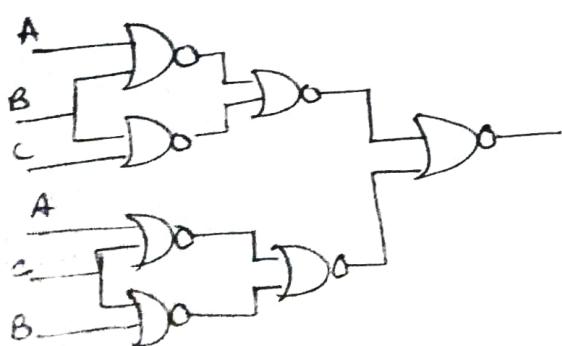(NOR-NOR) Example
what does following fn represents



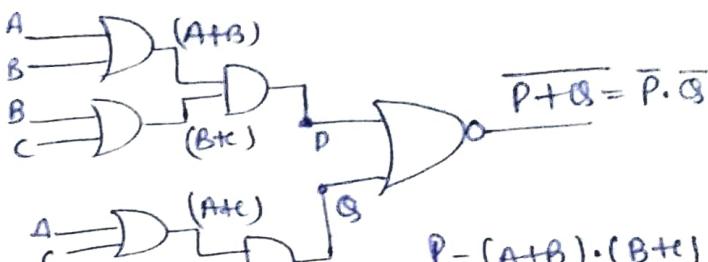Solⁿ (NOR-NOR) is same as (OR-AND) realisation.



$$\begin{aligned} P &= (A+B) \cdot (B+C) \\ &= \underline{B+AC} \end{aligned}$$

$$\begin{aligned} Q &= (A+B) \cdot (B+C) \\ &= \underline{C+AB} \end{aligned}$$

$$P \cdot Q = (\overline{B+AC}) \cdot (\overline{C+AB})$$

$$= \overline{B} \cdot (\overline{A+C}) \cdot \overline{C} (\overline{A}+\overline{B})$$

$$= (\overline{BA} + \overline{BC}) \cdot (\overline{CA} + \overline{CB})$$

$$\begin{aligned} &\Rightarrow \overline{B}\overline{A}C + \cancel{\overline{B}\overline{A}C} + \cancel{\overline{B}\overline{C}A} \xrightarrow[CC=0]{ZD} \\ &\quad + \cancel{\overline{B}\overline{C}B} \xrightarrow[CC=0]{ZD} \end{aligned}$$

$$\Rightarrow (\overline{AC} + \overline{C})(\overline{AB} + \overline{B})$$

⇒ $\overline{C}\overline{B}$ is the answer.


Q find the no. of 2 1/p eNOR gates require to represent

$$F(P,Q,R) = P+QR$$

Solⁿ (NOR-NOR) realisation (OR-AND)

So, find POS form of $P+QR$ is

$$(P+Q) \cdot (P+R)$$

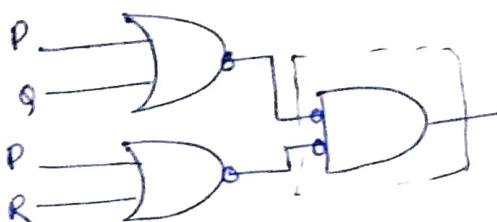

So, 3 NOR Gates are required.

Q Min. no of NOR gates required to implement

$$\begin{aligned} & x + x\bar{y} + x\bar{y}z \\ \Rightarrow & x + x\bar{y}(1+z) \\ \Rightarrow & x + x\bar{y} = x \end{aligned}$$

So, here no 'NOR' gates are required to implement.


→ Convert the expression into minimal form first.

→ We can implement using following ckt.



But we have no need to find b/w we require min. no. of NOR gates and its '0' b/w we can simple give x as input and x as output on no gate ckt.

Half Adder.

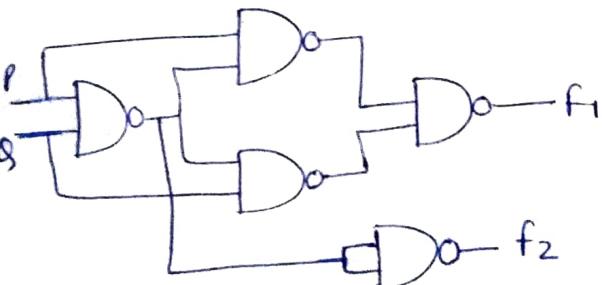


$$f_1 = P \oplus Q \quad (\text{Sum})$$

$$f_2 = PQ \quad (\text{Carry})$$

P	Q	f_1	f_2
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half adder adds 2 bits and full adder adds 3 bits.

Half Subtractor

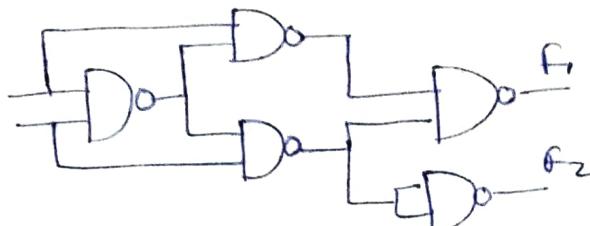


$$f_1 = P \oplus Q \quad (\text{Subtract})$$

$$f_2 = \overline{P}Q \quad (\text{Borrow})$$

P	Q	f_1	f_2
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

• $0 - 1 = 1$ with borrow b/w we can't 1 from 0 without borrow.

Comparator

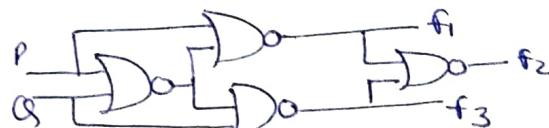

$$f_1 = \overline{P}Q \quad (P < Q)$$

$$f_2 = \overline{P}\overline{Q} + PQ \quad (P = Q)$$

$$f_3 = P\overline{Q} \quad (P > Q)$$


P	Q	f_2	f_1	f_3
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	0	0

Multiplexer (MUX)


→ A MUX is an electronic circuit that can connect one out of n^2 inputs to outputs.

→ MUX is a kind of switch.
 → It can't change the logical level of the input, it only provides the connection between I/p and O/p.

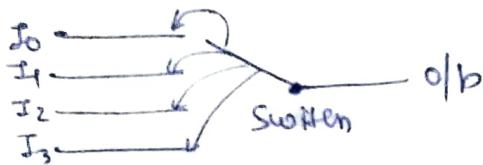→ It is functionally complete, i.e. all boolean functions can be realised using only multiplexers without any other gates.



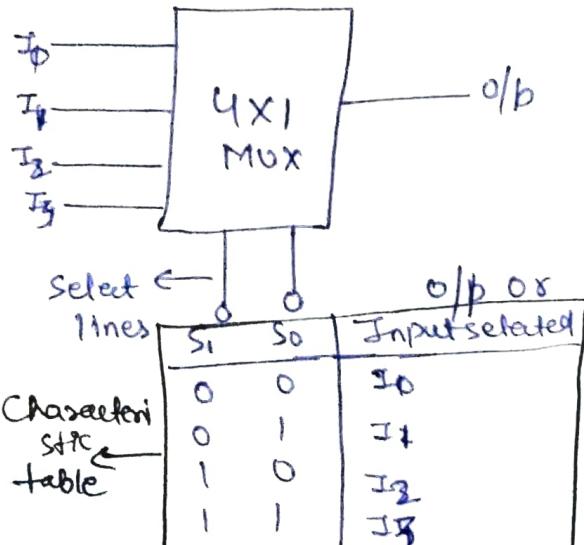You can connect switch with anyone of the I/p.




→ No. of select lines equals to 'n' if there are 2^n inputs.

→ Characteristic equation say O/p = f then,

$$f = \overline{S_1} \overline{S_0} I_0 + \overline{S_1} S_0 I_1 + S_1 \overline{S_0} I_2 + S_1 S_0 I_3$$

→ $2^n (2^n \times 1)$ MUX inputs = 2^n and select lines = n.

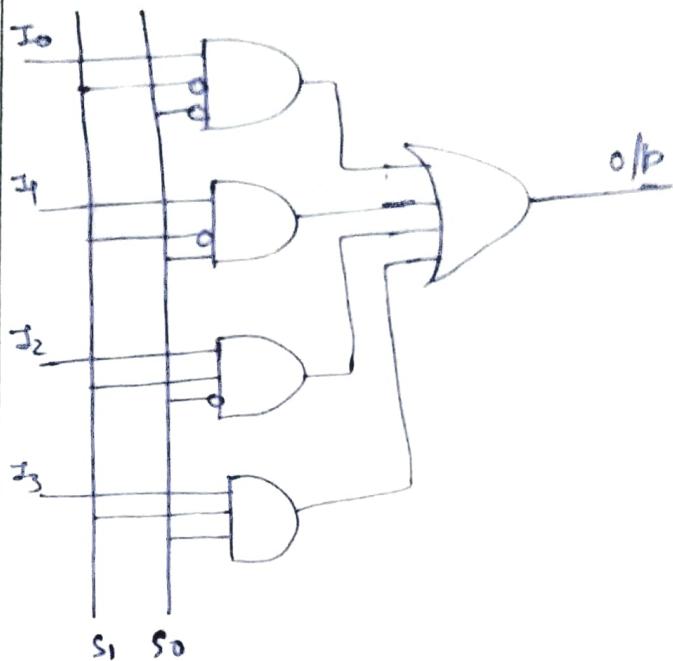AND-OR realisation for characteristic equation.



Note → MUX is functionally complete.

Implementation of function using MUX

Ex-1:

A	B	g
0	0	1
0	1	0
1	0	0
1	1	1

$$g(A, B) = \overline{A} \overline{B} \frac{(1)}{I_0} + \overline{A} B \frac{(0)}{I_1} + A \overline{B} \frac{(0)}{I_2} + A B \frac{(1)}{I_3}$$

Ex-2

A	B	h
0	0	1
0	1	0
1	0	1
1	1	0

If position A and B get interchanged then input will get changed.


→ If you have $(2^n \times 1)$ MUX
then you can implement
any function of n -variables.

Can we implement (8×1) MUX
using (4×1) MUX.

A	B	C	g
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


$$g = \overline{ABC} + \overline{ABC} + ABC \\ + ABC$$
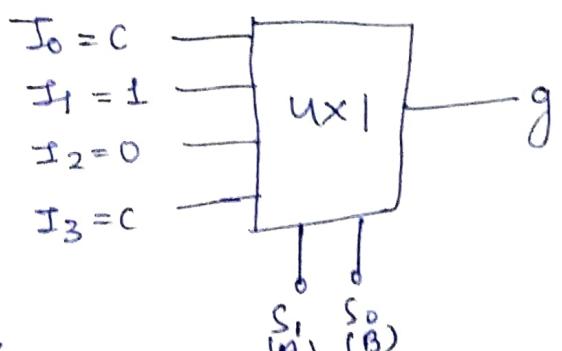
$$\Rightarrow \overline{A} \overline{B} \frac{(C)}{I_0} + A B \frac{(\overline{C} + C)}{I_1} \\ + A \overline{B} \frac{(0)}{I_2} + A B \frac{(C)}{I_3}$$



→ Using $(2^m \times 1)$ MUX we can
implement $(2^n \times 1)$ MUX
such that $m < n$ but you
need more number of gates.

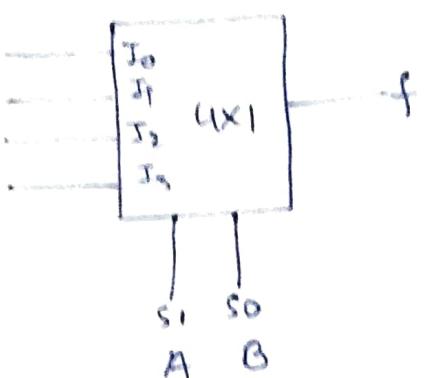Ex-3
 $f(A, B, C) = \Sigma(1, 2, 4, 6, 7)$




$$f = \overline{ABC} + ABC \\ + A\overline{B}\overline{C} + A\overline{B}C \\ + A\overline{BC}$$

$$\Rightarrow \overline{A} \overline{B} \frac{C}{I_0} + A B \frac{\overline{C}}{I_1} + A \overline{B} \frac{\overline{C}}{I_2} \\ + A B \frac{(C + \overline{C})}{I_3}$$


$$I_0 = C, \quad I_1 = \overline{C} = I_2, \quad I_3 = 1$$

MUX with Enable Input

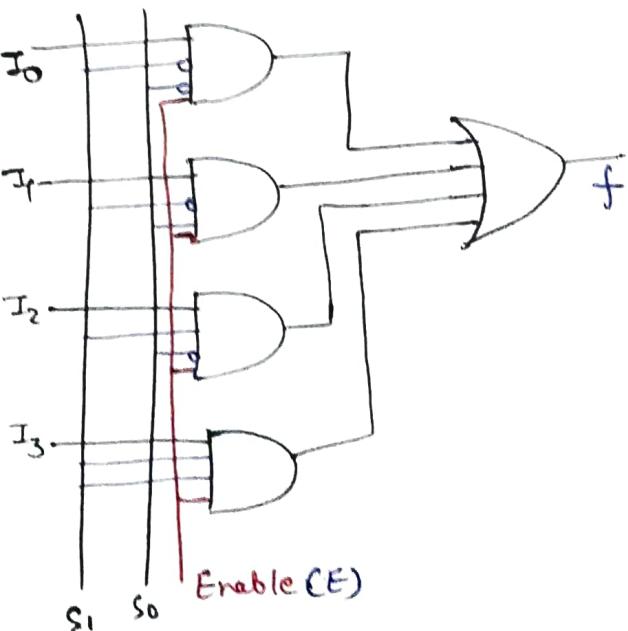

$$f = E(I_0 \overline{S}_1 \overline{S}_0 + I_1 \overline{S}_1 S_0 \\ + I_2 S_1 \overline{S}_0 + I_3 S_1 S_0)$$

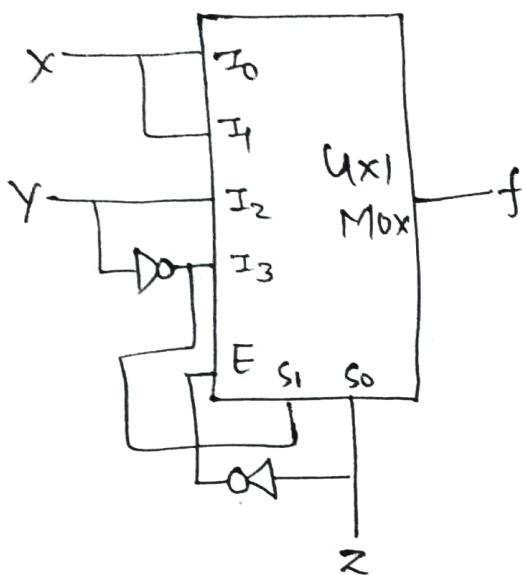Q) Minimize the function represented by following MUX.



$$f = E(I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0)$$

$$\Rightarrow f = (XY\bar{Z} + XYZ + Y\bar{Y}\bar{Z}^0 + \bar{Y}Z)\bar{Z}$$

$$\Rightarrow f = \bar{Z}(XY + \bar{Y}Z)$$

$$\Rightarrow f = XY\bar{Z}$$

~~Ques~~
Relation between select lines and input of MUX

$$f(A, B, C) = \Sigma(2, 3, 5, 6, 7)$$

a) $S_1 = B, S_0 = C$

b) $S_1 = C, S_0 = B$

use UX1 MUX. only.

a) $f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + ABC$

$$\Rightarrow (\bar{A}+A)\underbrace{\bar{B}\bar{C}}_{I_2} + (A+A)\underbrace{BC}_{I_3}$$

$$+ \underbrace{A\bar{B}C}_{I_1} + \underbrace{0\bar{B}\bar{C}}_{I_0}$$

$$I_0 = 0, I_1 = A, I_2 = I_3 = 1$$


b) $S_1 = C, S_0 = B$

$$I_0 = 0, I_1 = 1, I_2 = A, I_3 = 1$$

→ Input gets change according to select lines

Cascading MUX

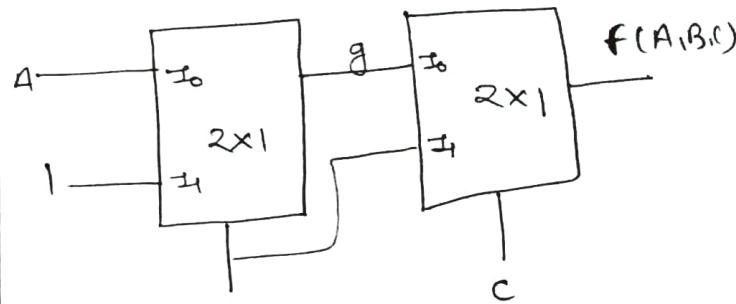Ex-1 What is the function in canonical SOP?



Sol'n

$$j = A\bar{B} + B$$


$$f = A\bar{B}\bar{C} + \bar{B}\bar{C} + BC$$

$$\Rightarrow A\bar{B}\bar{C} + B\bar{C}(A+\bar{A}) + BC(A+\bar{A})$$

$$\Rightarrow A\bar{B}\bar{C} + ABC\bar{A} + ABC + \bar{A}BC$$

$$f = \Sigma(4, 6, 2, 7, 3)$$

Ex-2

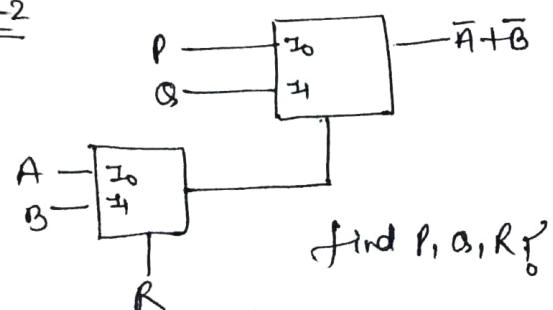

$$\text{find } P, Q, R$$


$$\text{SOL}^n (RA \cdot RB) P + (RN \cdot RB) Q$$

$$\Rightarrow (R \cdot A') \cdot (R' \cdot B') P + R \cdot N \cdot Q + R \cdot B \cdot Q$$

$$\Rightarrow R \cdot B' \cdot P + R' \cdot A' \cdot P + A' \cdot B' \cdot P + R' \cdot A \cdot Q$$

\Rightarrow We didn't give the option here but option should be given in the question. It is better to put the option in the last expression and verify.

Expansions of Multiplexers

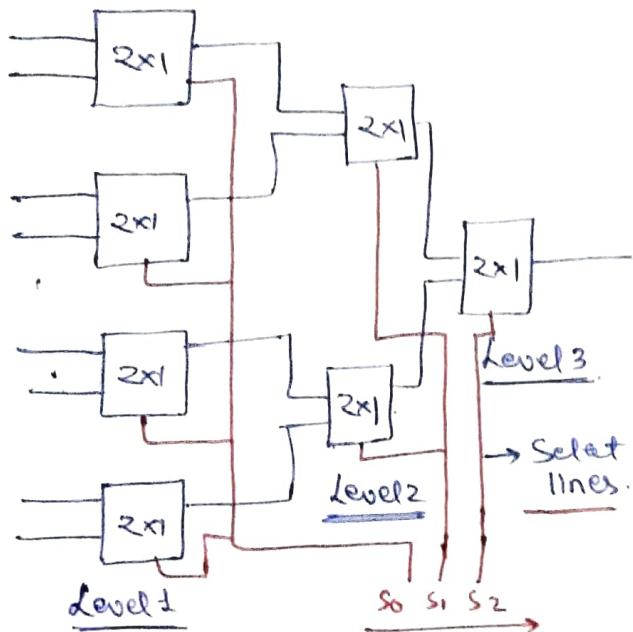

\rightarrow To construct a 8x1 MUX using 2x1 we need 7 MUX and 3 levels.

\rightarrow To develop a MX1 MUX using NX1 MUX we need,

① No. of levels (K) $\geq \log_N M$

Remember OR

$$K \geq \frac{\log_2 M}{\log_2 N}$$

In case of decimal values we can use ceil/floor function.

$$K = \lceil \log_N M \rceil$$

↳ In case of atleast

$$K = \lfloor \log_N M \rfloor \text{ in case of atmost}$$

② Total No. of devices require

$$D = \sum_{k=1}^{\lceil \log_2 M \rceil} (M/N^k)$$

③ At each level no. of device require -

$$[\text{at level } k = \frac{M}{N^k}]$$

\rightarrow Try to derive each formula by self. So that you can remember the logic behind this.

Ex → Implement 32x1 using 4x1.

$$\text{No. of level} = \lceil \log_4 32 \rceil = \lceil 2.5 \rceil = 3.$$

Device at levels

$$1 \rightarrow M/N = 8$$

$$2 \rightarrow M/N^2 = 2$$

$$3 \rightarrow M/N^3 = 1.$$


No. of device require

$$= 8 + 2 + 1 = 11.$$

Note →


Order of giving values to select lines is also important

Introduction to DEMUX

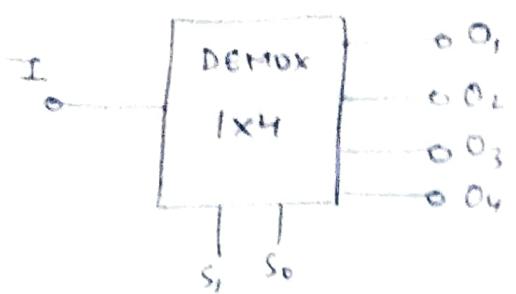


- It performs opposite operation of MUX.
- It has one input and 2^n outputs where 'n' is select lines.
- It is derived from MUX by joining all the inputs together and removing 'OR' gate.
- It is mainly used in the construction of switches.
- DEMUX is used as receiving end and MUX is used at transmitting ends.

Implementation of DEMUX

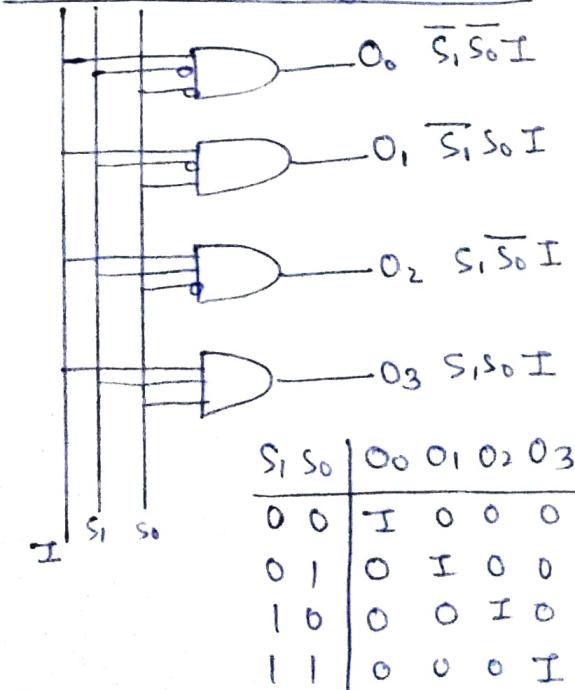

Characteristic equation represents output in terms of inputs



Ex → Switch using 2x1 MUX and 1x2 DEMUX

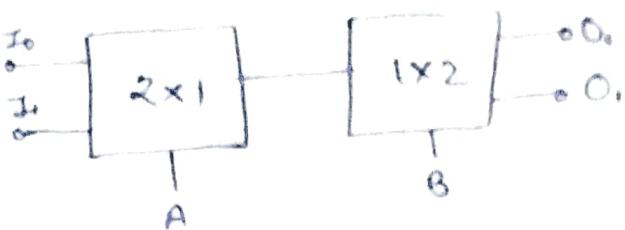


A	B	O ₀	O ₁	
0	0	I ₀	X	straight connection
0	1	X	I ₀	Cross connection (CC)
1	0	I ₁	X	
1	1	X	I ₁	

SC : I₀ on O₀ or I₁ on O₁.

CC : I₀ on O₁ or I₁ on O₀.

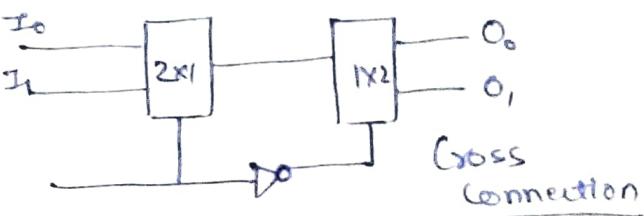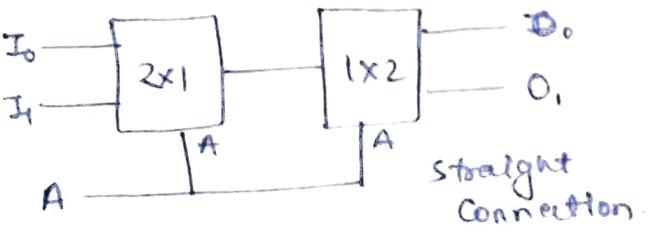

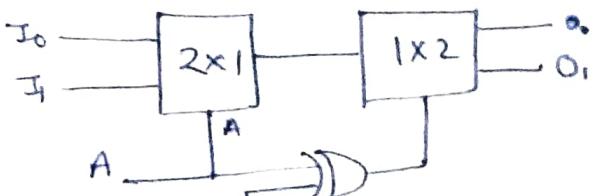
$$A \oplus 0 = A, \quad A \oplus 1 = \bar{A}$$



M = {0, 1} we can implement both SC or CC

Introduction to Decoder

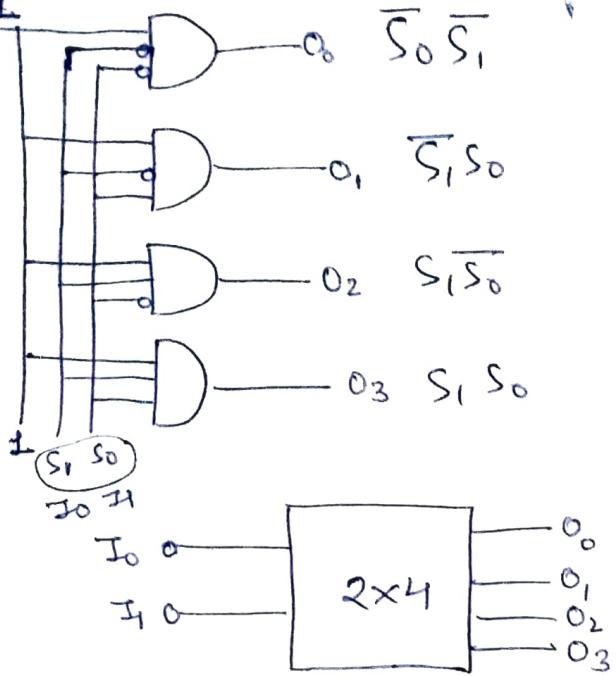

S ₁	S ₀	O ₀	O ₁	O ₂	O ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

→ A decoder is a device gives 2^n outputs for n inputs ($n \times 2^n$)


→ A demux can be converted to decoder by always setting $I=1$ and making select lines at inputs

→ Since a decoder provides all the minterms, we could implement any function in canonical SOP using "OR" gates

→ If all the 'AND' gates are replaced with 'NAND' gates, the decoder becomes active low.

→ In active low decoder we can implement any function in canonical SOP using NAND Gate.

Ex-1

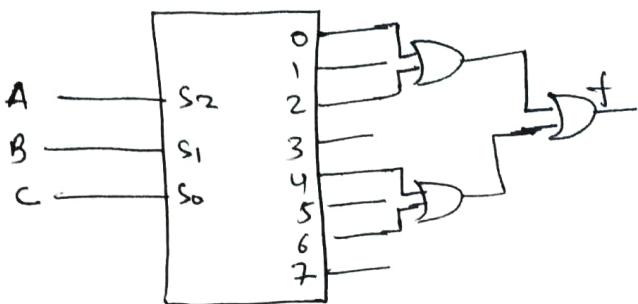


f is free from

- a) 1 variable
- b) two variable
- c) 3 variable
- d) None

Sol'n


$$f = \sum (0, 2, 4, 6)$$

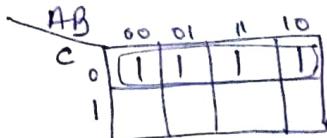

$f = \overline{C}$ independent of 2 variables.

→ A function with n-variables can be independent of all the n-variables if and only if all the cells of k-map is filled with 1 or all the cells are empty in case of SOP.

Ex-2

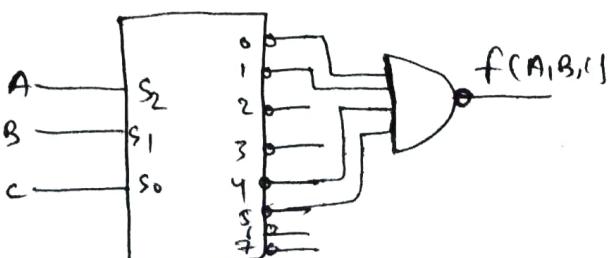

$f(A, B, C)$ is free from


- a) 1 variable b) 2 Variable
- c) 3 Variable d) 4 Variable

Solⁿ Given decoder is active low.


Say at, Q_0 input = \bar{ABC} and

$$0/p = (A+B+C)$$

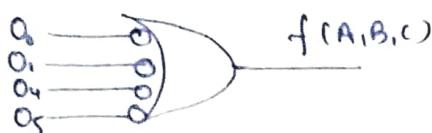→ Replace NAND with
Complemented OR Gate as



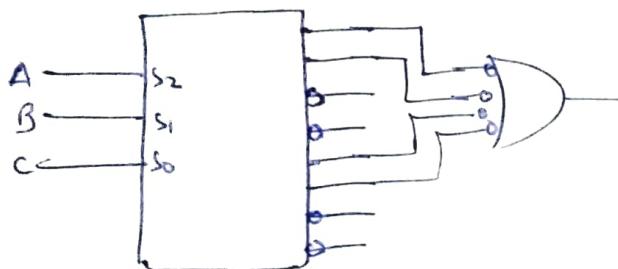If you use complemented 'OR'
gate then changes in fig.
Should be like,



$$f = \Sigma(0, 1, 4, 5)$$

	AB	00	01	11	10
C	0	1			1
	1	1			1

$$f = \bar{B} \text{ independent of } 2\text{-variables } (A, C).$$

Converting one code to another
using decoder.

Convert (8 4 2 1) Code to

(2 4 2 1) Code.

goto Note :-

8	11	2	1	2	11	2	1
A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0
2	0	0	1	0	0	0	1
3	0	0	1	1	0	0	1
4	0	1	0	0	0	1	0
5	0	1	0	1	1	0	1
6	0	1	1	0	1	1	0
7	0	1	1	1	1	1	0
8	1	0	0	0	1	1	0
9	1	0	0	1	1	1	1

Note → Just remember the method
of conversion, from here and
after this read about the
(8 4 2 1) and (2 4 2 1) code from
book.

Solⁿ

$$w = \Sigma(5, 6, 7, 8, 9) + \Sigma \phi(10-15)$$


$$x = \Sigma(4, 6, 7, 8, 9) + \Sigma \phi(10, 11, 12, 13, 14)$$

$$y = \Sigma(2, 3, 5, 8, 9) + \Sigma \phi(10, 11, 12, 13, 14)$$

$$z = \Sigma(1, 3, 5, 7, 9) + \Sigma \phi(10, 11, 12, 13, 14, 15)$$

→ Don't cares are same for all.

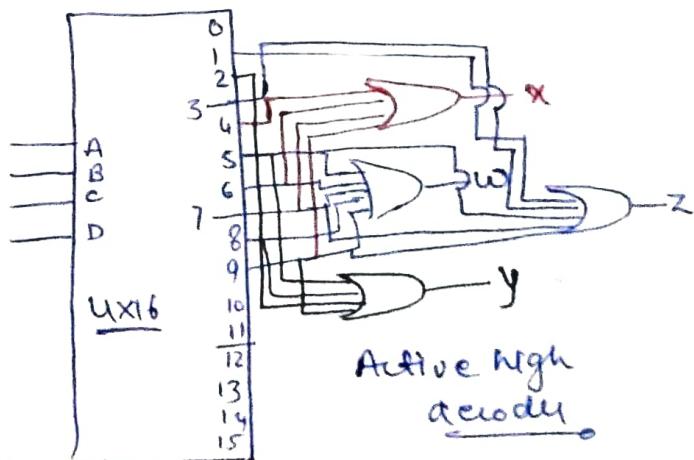for 9 0/p we need 4 variable
so, we need 4x16 decoder.



Active High
Decoder

ROM using decoder


- ROM can be used to realize combinational functions by storing appropriate values at appropriate locations.
- Every ROM is expressed in terms of ROM matrix and decoders.
- ROM matrix contains set of links and connections. The lines entering the matrix and leaving it are called, and the interaction of rows and columns are called as links.
- Decoder is a 'AND' realisation and we can implement a function using 'OR' Gate to perform (AND-OR) realisation.

Ex → Half Adder using connection and links

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \Sigma (1, 2)$$

$$C = \Sigma (3)$$

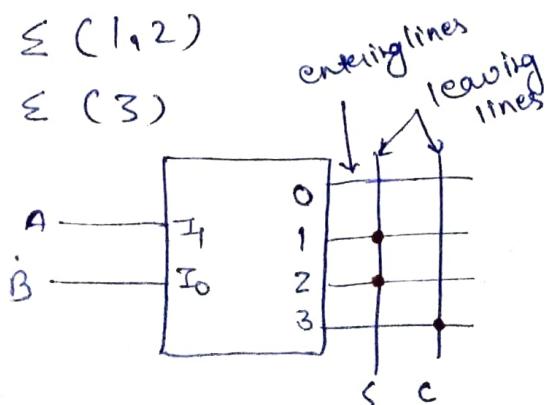


- 6 lines are connections
- 3 dots are links.
- Complete combination called as ROM.
- In ROM all the links are pre programmed if ROM get burns or destroyed all links get break down and it will not again fix down. So, ROM is not re-programmable.

→ ROM contain two things

- ① Decoder
- ② ROM matrix.

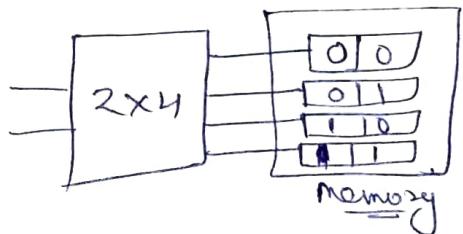→ ROM is a m/m bcoz it needs to remember about all the established links.



→ Horizontal lines chooses the address and vertical line selects the particular bit.

Use of decoder in implementing functions.

→ Each vertical line represent a function.

To implement a function with n variable we need of decode of size $(n \times 2^n)$.


If no. of function to implement is m then the total

no. of connections (lines)

$$\text{required} = [2^n + m] \text{ and}$$

$$\text{no. of links} = [2^n \times m]$$

Ex :

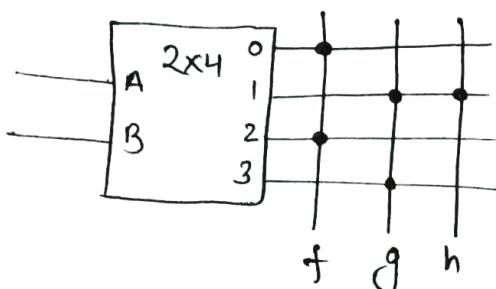

$$f(A, B) = \Sigma(0, 2)$$

$$g(A, B) = \Sigma(1, 3)$$

$$h(A, B) = \Sigma(1)$$


• No. of connection = 7 = 4+3

• links = $4 \times 3 = 12$

~~M~~ If M functions in N variables are need to implement then no. of links or size of ROM matrix is equals to $(2^N \times M)$

Implementing function using Decoder + MUX

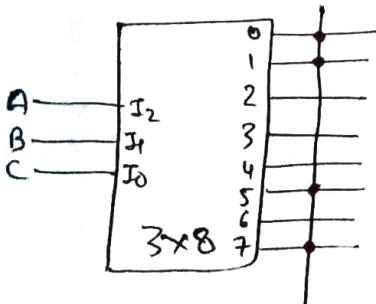Ex-1 How to decrease no. of connections in ROM matrix?




$$f(A, B, C) = \Sigma(0, 1, 5, 7)$$

$$\rightarrow f = A'B'C' + A'B'C + AB'C'$$

$$+ ABC$$

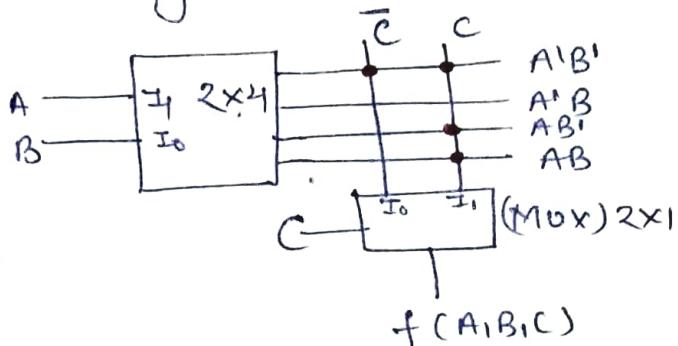Let's implement the same fn using 2x4 decoder




So, in above circuit we can implement the $f(A, B, C)$.


Here we need 6 connections and 8 links.

~~so~~ So, we can say that no. of connection can reduce but not links.

Ex-2

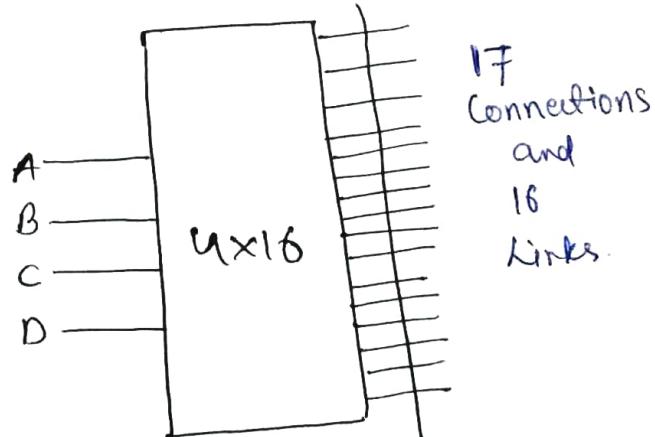


① Combination.

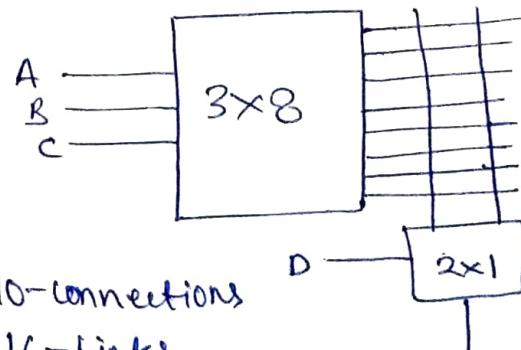

② Connection

8 connection
16 Links.

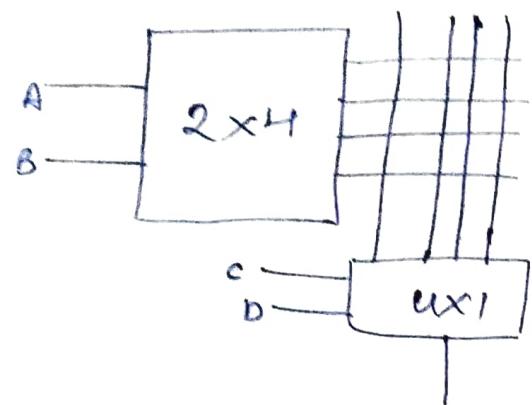


Solution


$$\begin{aligned}f &= AB + \bar{A} \\&= A(1+B) \\&= \underline{\underline{A}}\end{aligned}$$

Enable out
Direct multiply
OR IT F.Y

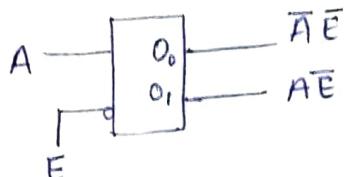→ Enable can be active high or active low.




Decoder with enable input

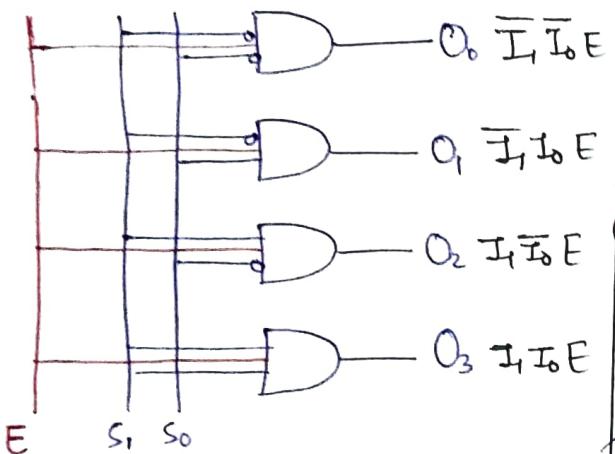


Instead of giving $E=1$ we can make it enable and give control to user.

Using enable signal we can expand the decoder.

Ex -

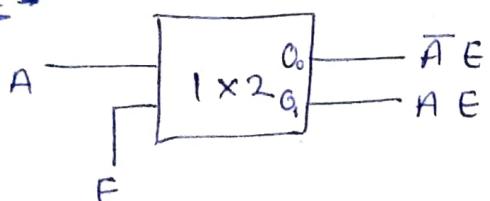

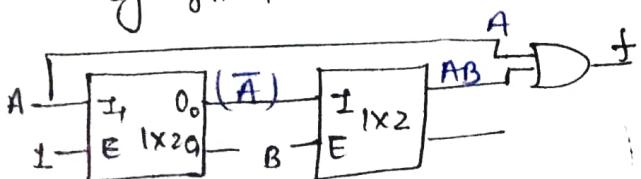③ find the function represented by given circuit.




I ₂	I ₁	I ₀	Output
0	0	0	O ₀
0	0	1	O ₁
1	1	1	O ₂
1	1	1	O ₃
1	1	1	O ₄
1	1	1	O ₅
1	1	1	O ₆
1	1	1	O ₇

function tables

Note: Must do it by self.


Construct a 2x4 decoder using 1x2 and construct its function tables.

6x64 Decoder using 3x8

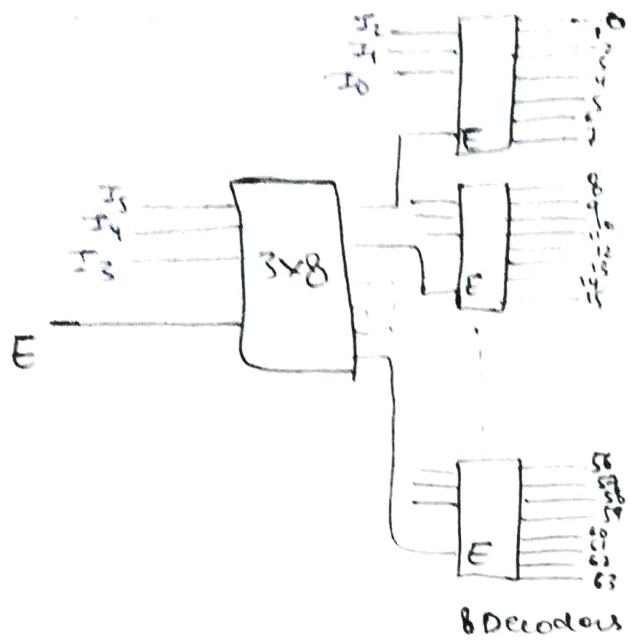

Assignment: To construct a 7x128 decoder using 3x8 decoders
Method:
Expansion of Decoder in another way:

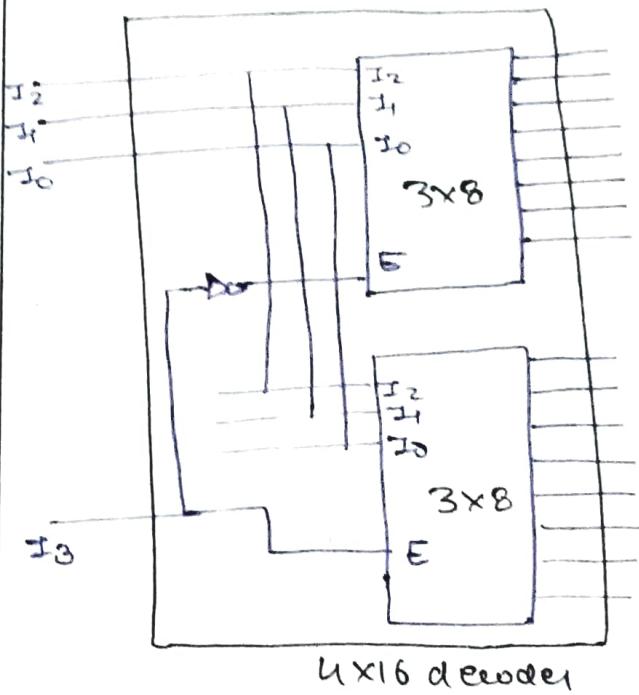Construction of 4x16 using two 3x8 decoders.



Expansion of decoder in general

We want to construct \$m \times 2^m\$ decoder using \$n \times 2^n\$ decoder or \$(\log m \times m)\$ decoder using \$(\log n \times n)\$ decoder. Then,

No. of levels required (\$K\$) is;

$$K \geq \log n^m$$

No. of device required (\$D\$) is;

$$D = \sum_{k=1}^{\log n^m} \left(\frac{m}{n^k} \right)$$

Ex → Construct a 6x64 decoder using 4x16.

$$\text{No. of levels} = \left\lceil \frac{\log 64}{\log 16} \right\rceil = \left\lceil \frac{6}{4} \right\rceil = 2$$

$$\text{No. of decoders} = \frac{64}{16} = 4 \text{ levels}$$

$$\text{A level 2} = \left\lceil \frac{8}{16} \right\rceil = 1$$

Total 9 decoders required

\$I_3	\$I_2	\$I_1	\$I_0	O/P
0	0	0	0	00
0	0	0	1	01
1	0	0	1	1
1	1	1	1	11
1	1	1	1	011

Construct a 5x32 decoder using 3x8 decoders and 2x4

